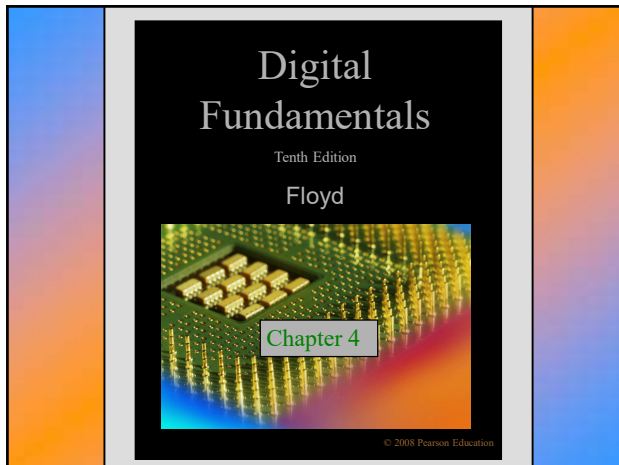




1

Summary

Karnaugh maps

The Karnaugh map (K-map) is a tool for simplifying combinational logic with 3 or 4 variables. For 3 variables, 8 cells are required (2^3).

The map shown is for three variables labeled A , B , and C . Each cell represents one possible product term.

Each cell differs from an adjacent cell by only one variable.

Floyd, Digital Fundamentals, 10th ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

2

Summary

Karnaugh maps

Cells are usually labeled using 0's and 1's to represent the variable and its complement.

The numbers are entered in gray code, to force adjacent cells to be different by only one variable.

Ones are read as the true variable and zeros are read as the complemented variable.

Floyd, Digital Fundamentals, 10th ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

3

Summary

Karnaugh maps

Alternatively, cells can be labeled with the variable letters. This makes it simple to read, but it takes more time preparing the map.

Example Read the terms for the yellow cells.

Solution
The cells are $\bar{A}\bar{B}\bar{C}$ and $\bar{A}B\bar{C}$.

Floyd, Digital Fundamentals, 10th ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

4

Summary

Karnaugh maps

K-maps can simplify combinational logic by grouping cells and eliminating variables that change.

Example Group the 1's on the map and read the minimum logic.

Solution

1. Group the 1's into two overlapping groups as indicated.
2. Read each group by eliminating any variable that changes across a boundary.
3. The vertical group is read $\bar{A}\bar{C}$.
4. The horizontal group is read $\bar{A}B$.

$X = \bar{A}\bar{C} + \bar{A}B$

Floyd, Digital Fundamentals, 10th ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

5

Summary

Karnaugh maps

A 4-variable map has an adjacent cell on each of its four boundaries as shown.

Each cell is different only by one variable from an adjacent cell.

Grouping follows the rules given in the text.

The following slide shows an example of reading a four variable map using binary numbers for the variables...

Floyd, Digital Fundamentals, 10th ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

6

Summary

Karnaugh maps

Example Group the 1's on the map and read the minimum logic.

Solution

1. Group the 1's into two separate groups as indicated.
2. Read each group by eliminating any variable that changes across a boundary.
3. The upper (yellow) group is read as $\overline{A}\overline{D}$.
4. The lower (green) group is read as AD .

$X = \overline{A}\overline{D} + AD$

Floyd, Digital Fundamentals, 10th ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

7

K-Maps > 4var

Material beyond this point will NOT be tested...information only

(added by D. Kohn)

Floyd, Digital Fundamentals, 10th ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved


8

5 Variable K-MAP (ver 1)

Floyd, Digital Fundamentals, 10th ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

9

5 Variable K-MAP (ver 2)

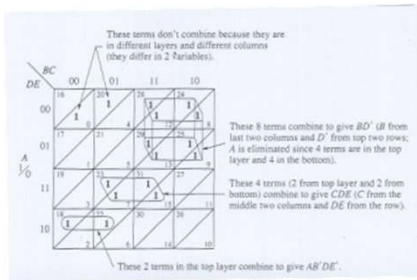
Floyd, Digital Fundamentals, 10th ed

© 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

10

6 Variable K-MAPS

(ver 2.0)

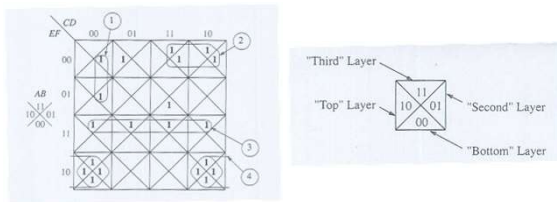Floyd, Digital Fundamentals, 10th ed

© 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

11

6 Variable or Greater

- There are a number of algorithms that allow minimization of digital logic circuits with any number of variables. Two of the most common are:
 - Quine-McCluskey
 - Espresso

Floyd, Digital Fundamentals, 10th ed

© 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

12
