



# Transmission Lines

TECH 3812  
Professor Kohn

THE UNIVERSITY OF  
MEMPHIS.

1

---

---

---

---

---

---


---

---

## Resistance and Resistivity

*For a wire of length  $l$  and cross-sectional area  $A$  the resistance  $R$ :*

- *Is proportional to  $l$*
- *And inversely proportional to  $A$*
- *The constant  $\rho$  (rho)*
- *Is known as the resistivity.*
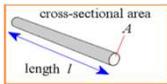
$$R = \rho \frac{l}{A}$$


THE UNIVERSITY OF  
MEMPHIS.

2

---

---

---

---

---

---

---


---

## Characterize the signal transferred between two modules

Unit A  
(source)

Unit B  
(receiver)

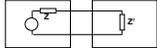Thevenin's theorem tells us that each unit can be modeled by voltage generator in series with an impedance



If we want to maximize the transfer of

- Current  $\rightarrow |Z'| \ll |Z|$
- Voltage  $\rightarrow |Z'| \gg |Z|$
- Power  $\rightarrow |Z'| = |Z|$

This is OK if the signals are slow and the system small

THE UNIVERSITY OF  
MEMPHIS.

3

---

---

---

---

---

---

---

---

### But with high speed signals

we have to consider the finite signal speed.  
 High speed signal lines are called transmission lines. They are often implemented as coaxial cables.



Each unit length  $dx$  of the transmission cable must have a capacitance  $dC/dx$ .  
 If we generate a  $v$  pulse at the time  $t=0$  it will propagate along the transmission line.  
 Each unit time a capacitor is charged with the charge  $Cv$  ( $C=Q/V$ )  
 Thus we need a constant current  $i=Cv/dt$   
 I.e. the transmission line behaves like an impedance with value  $Z=dV/dI$   
 $Z$  is the **characteristic impedance** of the cable



This is called **terminating** the finite transmission line so that it behaves like it was infinite

THE UNIVERSITY OF MEMPHIS

4

---

---

---

---

---

---

---

---

---

---

### Self Inductance

Self-inductance is usually just called inductance, symbolized by  $L$ .

Self-inductance is a measure of a coil's ability to establish an induced voltage as a result of a change in its current.

The induced voltage always opposes the change in current, which is basically a statement of Lenz's law.

The unit of inductance is the **henry (H)**. One henry is the inductance of a coil when a current, changing at a rate of one ampere per second, induces one volt across the coil.

THE UNIVERSITY OF MEMPHIS

5

---

---

---

---

---

---

---

---

---

---

### Lenz's Law

Recall Lenz's law states,

**When the current through a coil changes, an induced voltage is created across the coil that always opposes the change in current.**

In a practical circuit, the current can change because of a change in the load as shown in the following circuit example...

THE UNIVERSITY OF MEMPHIS

6

---

---

---

---

---

---

---

---

---


---

**Summary**

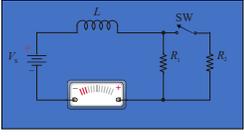**Lenz's law**

A basic circuit to demonstrate Lenz's law is shown.

Initially, the SW is open and there is a small current in the circuit through  $L$  and  $R_1$ .



THE UNIVERSITY OF MEMPHIS

7

---

---

---

---

---

---


---

---

**Summary**

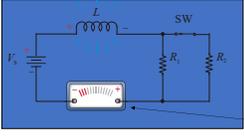**Lenz's law**

SW closes and immediately a voltage appears across  $L$  that tends to oppose any *change* in current.



Initially, the meter reads same current as before the switch was closed.

THE UNIVERSITY OF MEMPHIS

8

---

---

---

---

---

---


---

---

**Summary**

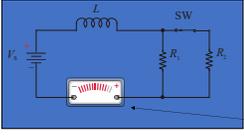**Lenz's law**

After a time, the current stabilizes at a higher level (due to  $I_L$ ) as the voltage decays across the coil.



Later, the meter reads a higher current because of the load change.

THE UNIVERSITY OF MEMPHIS

9

---

---

---

---

---

---

---

---

### Proximity Effect via Eddy Current

10

---

---

---

---

---

---

---

---

---

---

### Transmission Line Structures

11

---

---

---

---

---

---

---

---

---

---

### LC Measurement

12

---

---

---

---

---


---

---

---

---

---

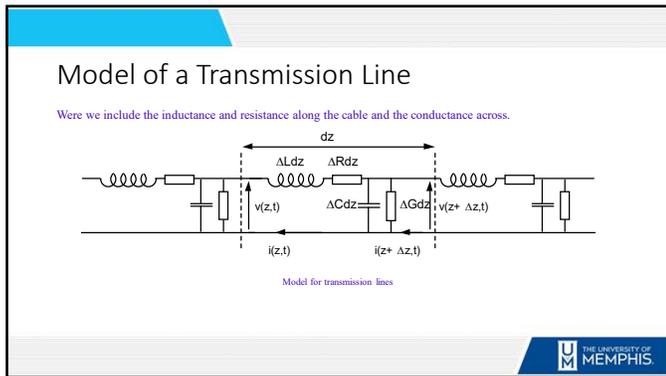

13

---

---

---


---

---

---

---

---

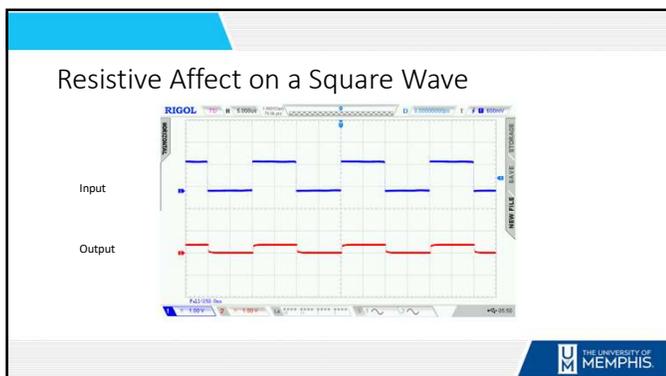

14

---

---

---


---

---

---

---

---

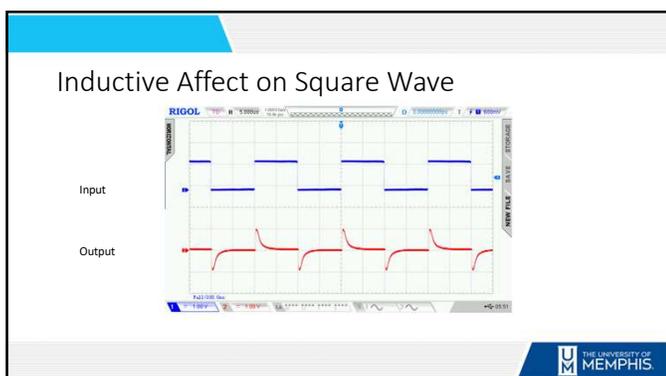

15

---

---

---


---

---

---

---

---

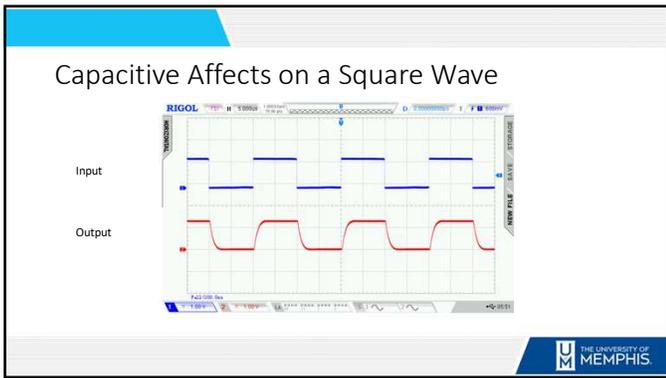

16

---

---

---

---

---

---

---

---

### Lab Demo

- See Lab #1

THE UNIVERSITY OF MEMPHIS

17

---

---

---

---

---

---

---

---